

Name:


Mission: **Circuit**

Date


Mission Code:

Circuits and electrical energy

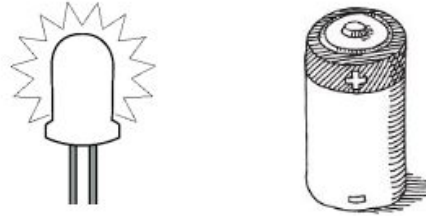Let's make light! Draw wires on the picture to show how you connected the light bulb to the battery.



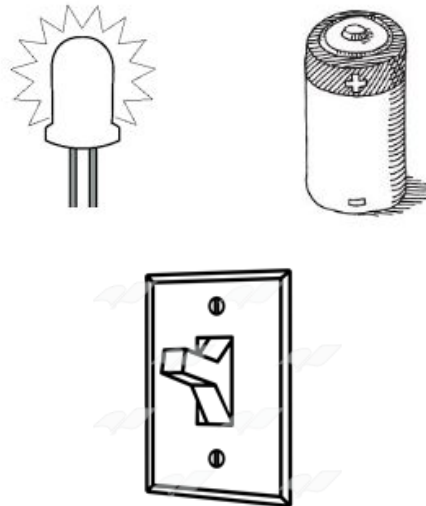
Let's add a switch: Draw wires on the picture to show how you connected the light bulb, the battery and the switch.



Fill in the blank with these words: connected, broken

When the switch is ON, the circuit is _____ and electricity flows. When the switch is OFF, the circuit is _____ and the electricity does not flow.

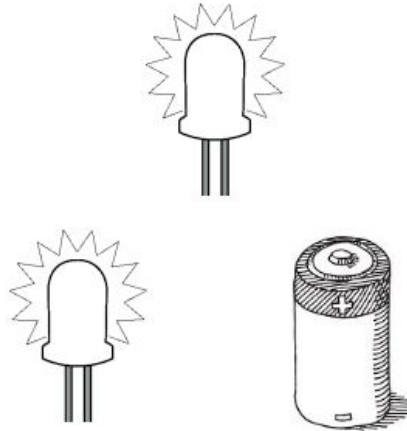Connect two lights: Draw wires on the picture to show how you connected the light bulbs to the battery.




How does the brightness change when you use two lights instead of one?

| Prediction | Observation |
|------------|-------------|
| | |

When there are two lights, the current is (circle one) *higher / lower* than when there is only one light. (circle one) *More / Less* energy is changed from electrical energy into light energy in each of the lights.

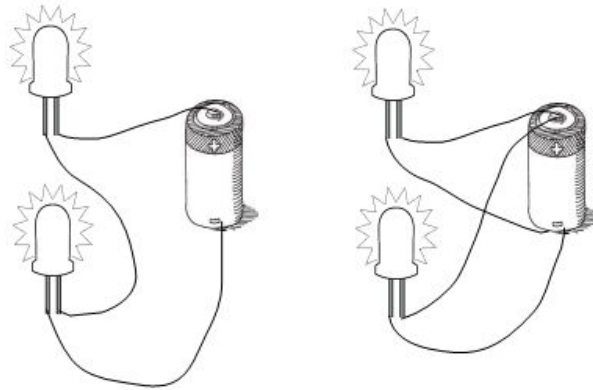Series and Parallel circuits: Make both of the circuits shown in the picture. Circle the one which lights up brighter.



Why does the circuit you circled have brighter light? Circle the correct reason:

The current is larger. The battery is stronger. The circuit is longer.

Mission completed stamp!

